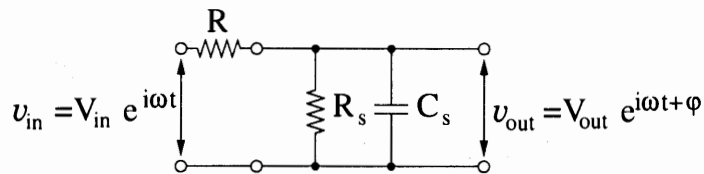


Name: \_\_\_\_\_

There are **two** questions to complete.

1.

(a) Determine the effective complex impedance  $Z_{||}$  of the parallel combination of  $R_s$  and  $C_s$ .

Now assume you can measure  $R_s$  and choose  $R$ , in the circuit shown above, such that  $R = R_s$ . Assume furthermore that you can measure and vary the frequency  $f$  of the input signal such that the magnitude of the capacitor's impedance equals the resistance,  $|Z_C| = R = R_s$ .

(b) Determine the ratio of the amplitudes  $V_{out}$  and  $V_{in}$ , i.e. the ratio of  $|v_{out}|$  and  $|v_{in}|$ .(c) What is the value of the capacitance  $C_s$  in terms of the measured quantities  $R$  and  $f$ ?

$$a) \quad Z_R = R_s ; \quad Z_C = \frac{1}{i\omega C_s} ; \quad \frac{1}{Z_{||}} = \frac{1}{Z_R} + \frac{1}{Z_C} = \frac{1}{R_s} + i\omega C_s = \frac{1 + i\omega R_s C_s}{R_s}$$

$$\hookrightarrow \boxed{Z_{||} = \frac{R_s}{1 + i\omega R_s C_s}} \quad \text{and} \quad |Z_{||}| = \frac{R_s}{\sqrt{1 + (\omega R_s C_s)^2}}$$

b) The circuit can be viewed as a voltage divider

$$\frac{|V_{out}|}{|V_{in}|} = \left| \frac{Z_{||}}{R + Z_{||}} \right|$$

Given  $R = R_s$  and  $f = f^*$  such that  $|Z_C| = \frac{1}{2\pi f^* C_s} = R$


$$\text{we get } Z_{||} = \frac{R}{1 + i}, \text{ therefore } \frac{|V_{out}|}{|V_{in}|} = \left| \frac{R/1+i}{R + \frac{R}{1+i}} \right| = \left| \frac{1}{2+i} \right| = \underline{\underline{\frac{1}{\sqrt{5}}}}$$

$$c) \quad \boxed{C_s = \frac{1}{2\pi f^* R}}$$

2.

$f^2 \text{ Hz}^2$	f (kHz)	$V_{out} \text{ (V)}$	$\left(\frac{10V}{V_{out}}\right)^2$
0	0	10.0	1
$1 \cdot 10^8$	10	10.0	1
$0.25 \cdot 10^{10}$	50	8.90	1.26
$1 \cdot 10^{10}$	100	7.11	1.98
$4 \cdot 10^{10}$	200	4.49	4.96
$9 \cdot 10^{10}$	300	3.16	10.0


$v_{in} = V_{in} \exp(i\omega t)$

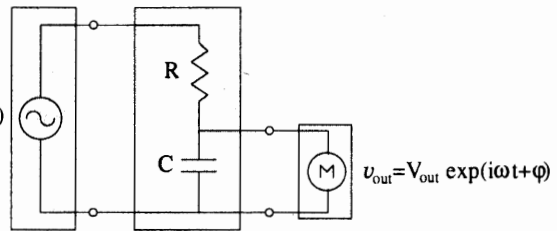

Given  $R = 1 \text{ k}\Omega$  and  $V_{in} = 10 \text{ V}$ , graph the above data on a straight line plot and determine the value of the capacitance  $C$ .

Voltage divider with  
 $z_1 = R$      $z_2 = \frac{1}{i\omega C}$

$$\frac{V_{out}}{V_{in}} = \left| \frac{z_2}{z_1 + z_2} \right| = \left| \frac{1/i\omega C}{R + 1/i\omega C} \right| = \frac{1}{|\omega RC + 1|} = \frac{1}{\sqrt{(\omega RC)^2 + 1}}$$

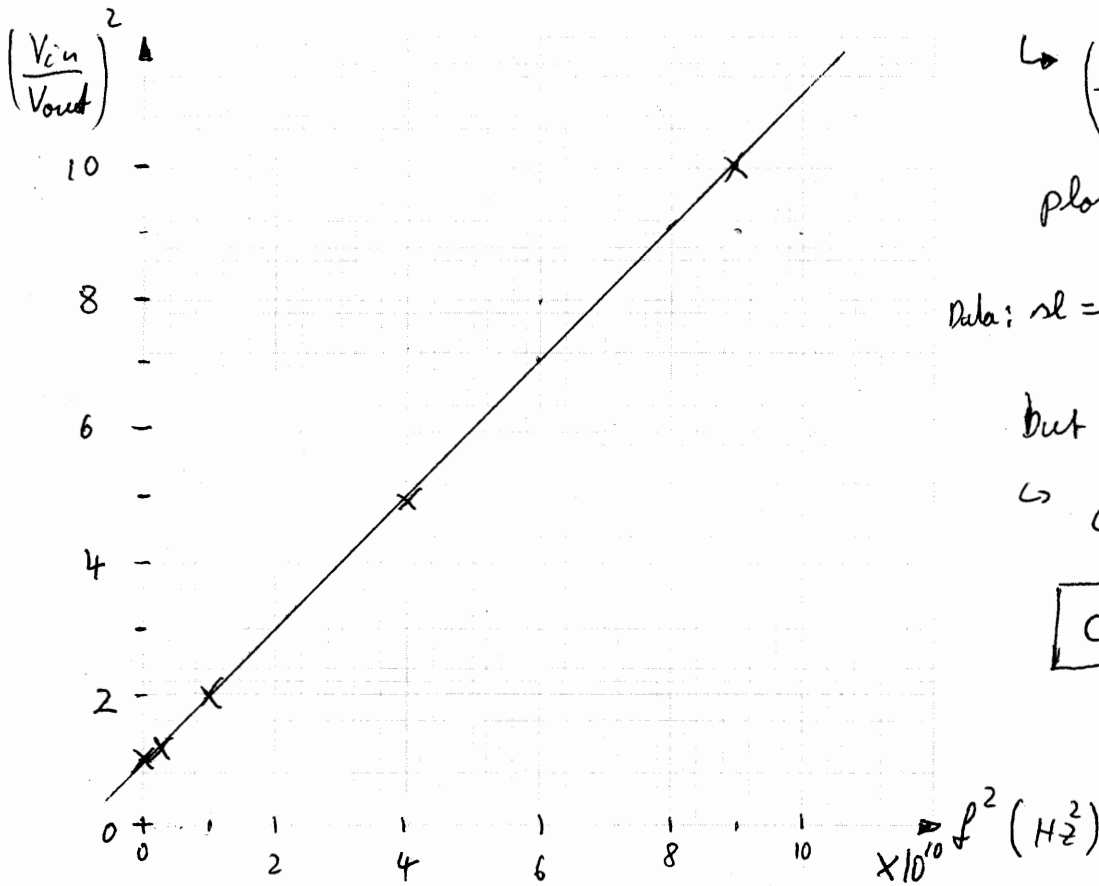

$$\hookrightarrow \left(\frac{V_{in}}{V_{out}}\right)^2 = 1 + (2\pi RC)^2 \cdot f^2$$

plot  $\left(\frac{V_{in}}{V_{out}}\right)^2$  vs.  $f^2$

Data:  $sl = \frac{[10 - 1]}{9 \cdot 10^{10} \text{ Hz}^2} = 1 \cdot 10^{-10} \text{ s}^2$

but  $sl = (2\pi RC)^2$

$$\hookrightarrow C = \frac{\sqrt{sl}}{2\pi R} = \frac{1 \cdot 10^{-5} \text{ s}}{2\pi \cdot 1 \cdot 10^3 \Omega}$$

**$C \approx 1.6 \text{ nF}$**