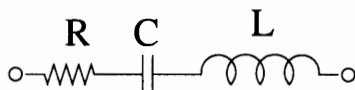


Name: _____

There are **three questions** to complete.

1. Determine the magnitude $|Z|$ of the total impedance Z of the following circuit



What are the limits on your expression for $|Z|$ as the angular frequency ω approaches 0 and ∞ ? Can you explain these limits intuitively?

$$Z = Z_R + Z_C + Z_L = R + \frac{1}{i\omega C} + i\omega L = R + i\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\omega \rightarrow 0$$

$$|Z| \rightarrow \infty$$


capacitor blocks current flow

$$\omega \rightarrow \infty$$

$$|Z| \rightarrow \infty$$

inductor chokes off the current flow

2.

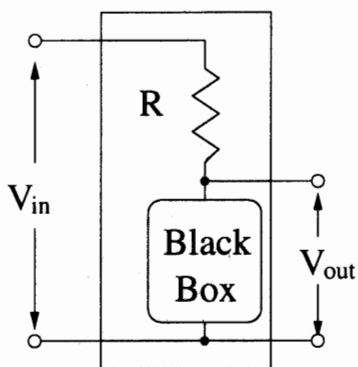


Plot qualitatively the expected behavior of V_{out} as a function of the input frequency f [$v_{in} = V_{in} \cos(2\pi ft)$] if the black box contains


- (a) a resistor,
- (b) an inductor,
- (c) a capacitor,
- (d) an inductor and capacitor in parallel,
- (e) an inductor and capacitor in series.

In general, the gain is $g = \frac{V_{out}}{V_{in}} = \left| \frac{Z}{R+Z} \right|$. For fixed V_{in} , $g \propto V_{out}$. Plot g , $g \in [0, 1]$


a) $Z = r \quad g = \frac{r}{R+r}$

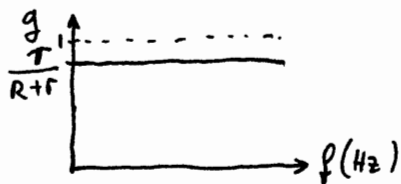

b) $Z = i\omega L \quad g = \left| \frac{i\omega L}{R+i\omega L} \right| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}}$

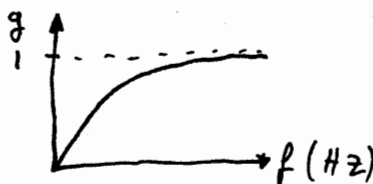


c) $g = \left| \frac{1/i\omega C}{R + 1/i\omega C} \right| = \left| \frac{1}{i\omega RC + 1} \right| = \frac{1}{\sqrt{\omega^2 R^2 C^2 + 1}}$

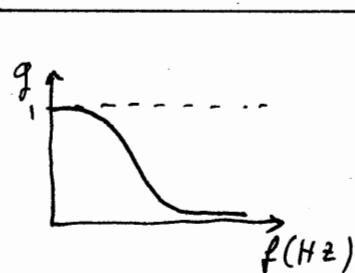

d) $Z = \frac{Z_L \cdot Z_C}{Z_L + Z_C} = \frac{i\omega L \cdot \frac{1}{i\omega C}}{i\omega L + \frac{1}{i\omega C}} = (-i) \frac{L/C}{(\omega L - \frac{1}{\omega C})}$

$ Z = \left \frac{L/C}{\omega L - \frac{1}{\omega C}} \right $	$\omega \rightarrow 0$	$\omega \rightarrow \infty$	$\omega \rightarrow \frac{1}{\sqrt{LC}}$
	0	0	∞


$g = \left \frac{Z}{R+Z} \right $	0	0	1
------------------------------------	---	---	---

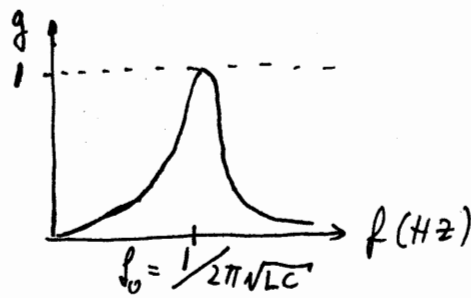


e) $Z = Z_L + Z_C = i\omega L + \frac{1}{i\omega C} = i(\omega L - \frac{1}{\omega C})$

$ Z = \left \omega L - \frac{1}{\omega C} \right $	$\omega \rightarrow 0$	$\omega \rightarrow \infty$	$\omega \rightarrow \frac{1}{\sqrt{LC}}$
	∞	∞	0

$g = \left \frac{Z}{R+Z} \right $	1	1	0
------------------------------------	---	---	---

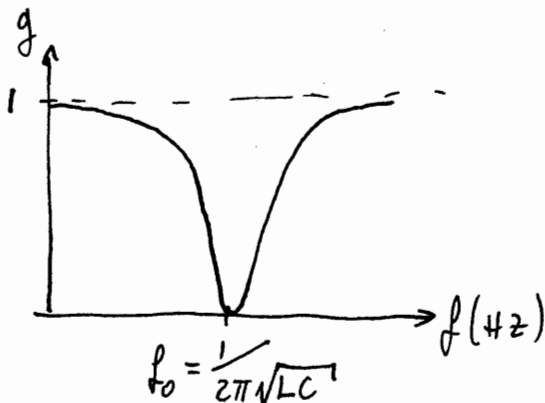

3.

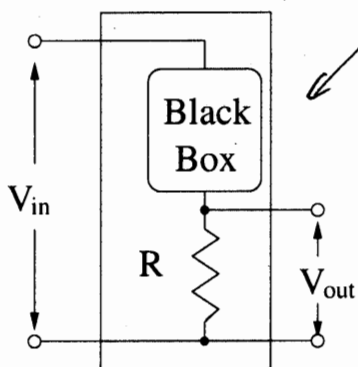

note, the B.B. is on top and V_{out} is measured across R !

For a black box containing a capacitor C and an inductor L that are connected in series, derive the resonance frequency f_0 and the FWHM (full-width-half-maximum) value Δf of the resonance peak that is seen when plotting $|v_{out}|^2/|v_{in}|^2 = V_{out}^2/V_{in}^2$. Give your answer in terms of L, C , and R .

$$Z = Z_L + Z_C = i\omega L + \frac{1}{i\omega C} = i\left(\omega L - \frac{1}{\omega C}\right)$$

$$\frac{|V_{out}|^2}{|V_{in}|^2} = \left| \frac{R}{R + Z} \right|^2 = \frac{R^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

1) Find resonance freq. f_0 :

Method A: Guess that $\omega_0 = \frac{1}{\sqrt{LC}}$. Then $\frac{|V_{out}|^2}{|V_{in}|^2} = \frac{R^2}{R^2 + 0} = 1$, which we know is the maximum possible gain for a passive-element circuit such as this one. So our guess must be correct.

Method B: Find max. of $(V_{out}/V_{in})^2$, or min. of $(V_{in}/V_{out})^2$, formally:

$$0 = \frac{d}{d\omega} \left(\frac{V_{in}}{V_{out}} \right)^2 = \frac{d}{d\omega} \left(1 + \frac{1}{R^2} \left[\omega L - \frac{1}{\omega C} \right]^2 \right) = \frac{2}{R} \left(\omega L - \frac{1}{\omega C} \right) \left(L + \frac{1}{\omega^2 C} \right)$$

$$\hookrightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ only solution in } \mathbb{R}$$

$$\Rightarrow \boxed{f_0 = \frac{1}{2\pi\sqrt{LC}}}$$

2) Find FWHM:

$$\frac{1}{2} = \left(\frac{V_{out}}{V_{in}} \right)^2 = \frac{R^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \rightarrow \text{Solve } \left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\text{That is: } \omega_{\pm} L - \frac{1}{\omega_{\pm} C} = \pm R \quad \left| \cdot \frac{\omega_{\pm}}{L} \right.$$

$$\hookrightarrow \omega_{\pm}^2 \mp \omega_{\pm} \frac{R}{L} - \frac{1}{LC} = 0$$

The two real and positive solutions are (one for ω_+ and one for ω_-)

$$\omega_+ = +\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \quad \omega_- = -\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\hookrightarrow \Delta\omega = \omega_+ - \omega_- = \frac{R}{L}$$

$$\boxed{\Delta f = \frac{R}{2\pi L}}$$