

Name: _____

1. Determine an expression for the gain $g = \frac{V_{out}}{V_{in}}$ of the non-inverting amplifier shown in Fig. 1. The triangles indicate the ground (0 V) level, relative to which V_{in} and V_{out} are measured.

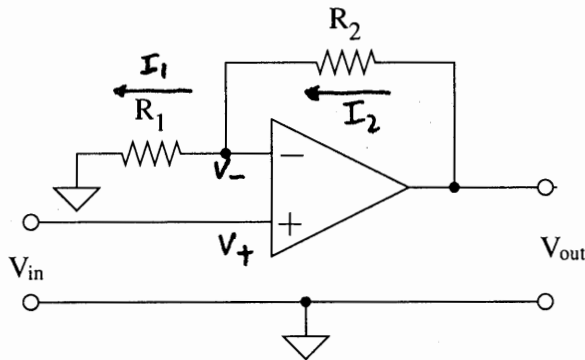


Figure 1: Non-inverting amplifier

Using the Golden Rules

$$\text{GRI: } V_- = V_+ = V_{in}$$

$$\text{GRII: } I_2 = I_1$$

use Ohm's law for the currents I_2, I_1

$$\frac{V_{out} - V_-}{R_2} = \frac{V_-}{R_1}$$

$$\frac{V_{out} - V_{in}}{R_2} = \frac{V_{in}}{R_1}$$

$$\hookrightarrow V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$g = 1 + \frac{R_2}{R_1}$$

2.

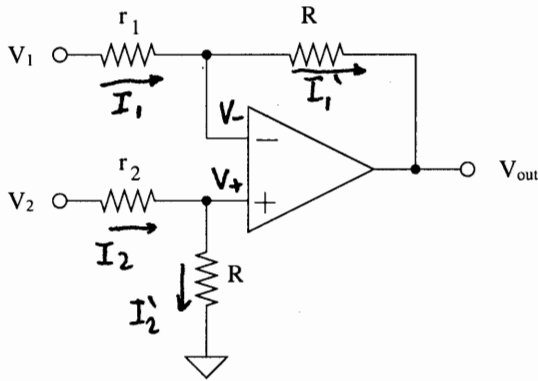


Figure 2: "Making a difference"

For $r_1 = r_2 = r$, the circuit on the left has an output that is the amplified voltage difference of its inputs.

$$V_{out} = \frac{R}{r} (V_2 - V_1)$$

However, measuring differences can be difficult as you will show in this and the next problem.

Show that for $r_1 \neq r_2$

$$V_{out} = \left(\frac{r_1 + R}{r_2 + R} \frac{R}{r_1} \right) V_2 - \frac{R}{r_1} V_1.$$

Use the Golden Rules for op-amps:

$$\text{GRI: } V_- = V_+$$

$$\text{GRII: } I_1 = I_1'$$

$$I_2 = I_2'$$

use Ohm's law $I_1 = I_1' \rightarrow \frac{V_1 - V_-}{r_1} = \frac{V_- - V_{out}}{R} \rightarrow V_{out} = V_- - \frac{R}{r_1} (V_1 - V_-)$

$$V_+ = V_-; I_2 = I_2' \rightarrow \frac{V_2 - V_-}{r_2} = \frac{V_-}{R} \rightarrow V_2 = V_- \left(1 + \frac{r_2}{R} \right)$$

$$\hookrightarrow V_- = V_+ = V_2 \frac{R}{r_2 + R}$$

$$\Rightarrow V_{out} = V_2 \frac{R}{r_2 + R} \left(1 + \frac{R}{r_1} \right) - \frac{R}{r_1} V_1$$

$$V_{out} = \left(\frac{r_1 + R}{r_2 + R} \frac{R}{r_1} \right) V_2 - \frac{R}{r_1} V_1$$

3. Continuing with the circuit shown in Fig. 2, consider a situation where you were able to pick resistors such that $R = r_1 = r$ holds exactly, so that the resistor values ($= r$) have a standard deviation $\sigma = 0$. In contrast, for r_2 you just took a resistor from the bin, so there is an uncertainty σ_r , i.e. $r_2 = r \pm \sigma_r$.

a) Derive an expression for the resulting error term σ_Δ : $V_{out} = \Delta = (V_2 - V_1) \pm \sigma_\Delta$.

b) In lab we use 5% resistors ($\sigma_r/r = 5\%$). If $V_2 = 10$ V, what is the minimum voltage difference $|\Delta| = |V_2 - V_1|$ for which the resulting relative measurement uncertainty is better than 10% ($\sigma_\Delta/|\Delta| < .1$)?

$$a) \text{ From 2: } V_{out} = \frac{r_1 + R}{r_2 + R} \frac{R}{r_1} V_2 - \frac{R}{r_1} V_1 \underset{\substack{\uparrow \\ r=R=r_1}}{=} \frac{2r}{r_2 + r} V_2 - V_1 \underset{\substack{\uparrow \\ r_2=r}}{=} V_2 - V_1 = \Delta$$

To keep track of errors define $x = r \pm 0$ and $y = r_2 = r \pm 6r$. We want to know the absolute uncertainty σ_Δ of

$$\Delta(x, y) = \frac{2x}{x+y} V_2 - V_1 \quad \text{where } x = y = r$$

$$\text{From handout: } \sigma_\Delta = \sqrt{\left(\frac{\partial \Delta}{\partial x}\right)^2 (\sigma_x)^2 + \left(\frac{\partial \Delta}{\partial y}\right)^2 (\sigma_y)^2} = \left|\frac{\partial \Delta}{\partial y}\right| \sigma_r$$

$$\frac{\partial \Delta}{\partial y} \Big|_{x=y=r} = \frac{-2x}{(x+y)^2} V_2 \Big|_{x=y=r} = -\frac{V_2}{2r} \rightarrow \boxed{\sigma_\Delta = \frac{\sigma_r V_2}{2r}}$$

$$b) \frac{\sigma_r}{r} = 5\%; \text{ Want } \frac{\sigma_\Delta}{|\Delta|} < 10\%$$

$$\hookrightarrow \frac{\sigma_r}{r} \frac{V_2}{2} < 10\% |\Delta| \rightarrow \frac{5\%}{10\%} \frac{10V}{2} < |\Delta| \rightarrow \boxed{|\Delta| > 2.5V}$$

If the voltage difference at the two input ports falls below 25% of V_2 , the measurement uncertainty becomes unacceptable. Unless the resistors are matched precisely, this is a terrible circuit for measuring $V_2 - V_1$. There exist special circuits called "Instrument Amplifiers" that are designed for the purpose of measuring $V_2 - V_1$ with good precision.