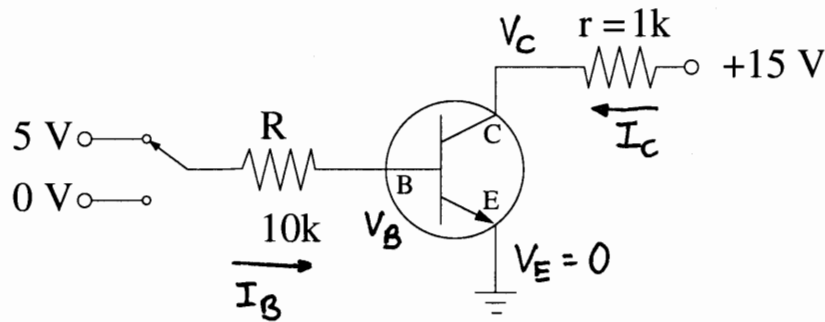


Name: _____

1. Calculate the current through the resistor r in the transistor switch shown below when the input is set to 5 V.



Since we are considering switches it is reasonable to assume that the transistor is saturated. If saturated $V_c \approx 0.2V$ and, therefore,

$$I_c = \frac{15V - 0.2V}{r} = \frac{14.8V}{1 \cdot 10^3 \Omega} = 14.8 \text{ mA} \quad (= I_c^{\max})$$

We now have to check our assumption:

We know that $V_B \approx 0.6V$


$$\hookrightarrow I_B = \frac{5V - 0.6V}{R} = \frac{4.4V}{10 \cdot 10^3 \Omega} = 0.44 \text{ mA}$$

Thus, for $\beta \geq 100$ $\beta I_B > I_c^{\max} \approx 15 \text{ mA}$

\hookrightarrow Our assumption is correct, the transistor is in the saturated regime.

$$I_c = 14.8 \text{ mA}$$

2.

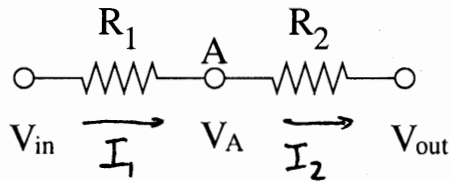

For the voltage divider shown on the left, prove that the voltage V_A at point A is given by

$$V_A = \frac{V_{in} R_2 + V_{out} R_1}{R_1 + R_2}$$

Kirchhoff's current law: $I_1 = I_2$

Ohm's law: $I_1 R_1 = V_{in} - V_A$; $I_2 R_2 = V_A - V_{out}$

$$\hookrightarrow V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} \quad | \cdot \frac{R_1 R_2}{R_1 + R_2}$$

$$\boxed{V_A = \frac{V_{in} R_2 + V_{out} R_1}{R_1 + R_2}}$$

When incorporated into a Schmitt Trigger, V_{out} can only take on two possible values: 0 ("low") and V_{DD} ("high"). A change in the output can only occur when the voltage V_A crosses through a threshold voltage V_T . Show that if the output is low, the input voltage required to switch to the high state is

$$V_{low-to-high} = \frac{(R_1 + R_2) V_T}{R_2}$$

while, if the output is high, the input voltage required to switch to the low state is

$$V_{high-to-low} = -\frac{R_1 V_{DD}}{R_2} + \frac{(R_1 + R_2) V_T}{R_2}$$

Thus, the hysteresis of a Schmitt Trigger is given by


$$\Delta V = V_{low-to-high} - V_{high-to-low} = \frac{R_1 V_{DD}}{R_2}$$

low-to-high: ($V_{in} := V_{L \rightarrow H}$)

$V_A := V_T$ and $V_{out} = 0$ (start low)

$$V_T = \frac{V_{L \rightarrow H} \cdot R_2 + 0 \cdot R_1}{R_1 + R_2}$$
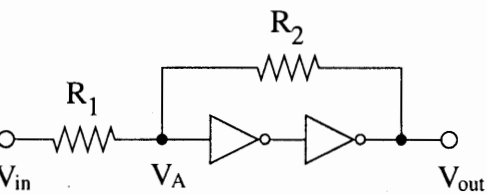
$$\hookrightarrow \boxed{V_{L \rightarrow H} = \frac{R_1 + R_2}{R_2} V_T}$$



Schmitt trigger circuit

high-to-low: ($V_{in} := V_{H \rightarrow L}$)

$V_A := V_T$ and now $V_{out} = V_{DD}$ (start high)

$$V_T = \frac{V_{H \rightarrow L} \cdot R_2 + V_{DD} \cdot R_1}{R_1 + R_2}$$

$$\hookrightarrow \boxed{V_{H \rightarrow L} = -\frac{R_1}{R_2} V_{DD} + \frac{R_1 + R_2}{R_2} V_T}$$

$$\boxed{\Delta V = V_{L \rightarrow H} - V_{H \rightarrow L} = \frac{R_1}{R_2} V_{DD}}$$